

# Digital Logic Circuit Simulator

Group Members:

Meghanad Shingate (09307608)

Nirbhay Rane (09307905)

Bharat Kumar (09307904)

Group : 13

AE663 Final Presentation

(Google code repository - <http://code.google.com/p/pydlcs/>)

November 28, 2011

## Implementation of Logic Circuit Simulator using Python

- Basic logic gates (e.g. AND, OR, NOR, etc.)
- Combinational Logic circuits (e.g. Half adder, Full adder, Mux/Demux etc.)
- Sequential Logic circuits (e.g Flip-Flop, Counters, Shift registers etc.)
- Digital signal sources ( e.g. clock source)
- Simulation of any circuit designed using above elements

# Implementation Details - Class Structure

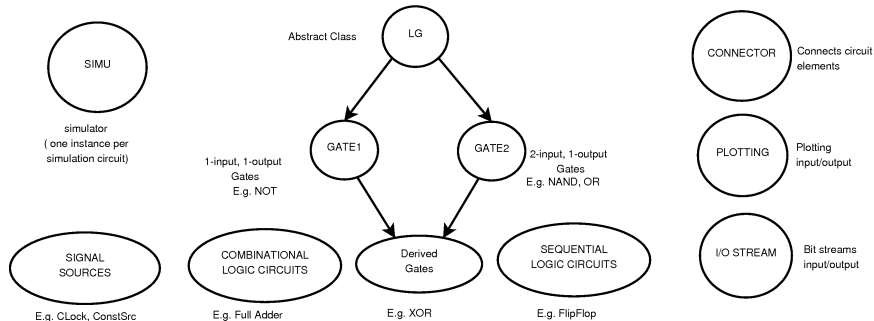


Figure: Class Structure

# Implementation Details - Simulator Model

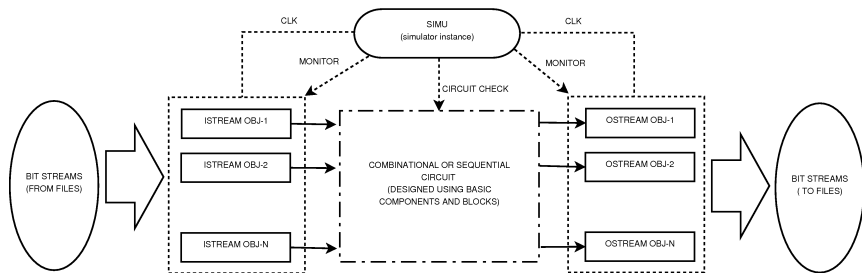


Figure: Simulator model

# Implementation Details - Simulator Model

 


Figure: *SIMU* Class details

 


Figure: *i/o stream* model

## Logic Gate Class - Abstract Class

```
1 # CLASS : LOGIC GATE (LG)
2 class LG :
3     def __init__ (self, name) :
4         self.name = name
5     def evaluate (self) : return
```

## Logic Gate Class - Abstract Class

```
1 # CLASS : LOGIC GATE (LG)
2 class LG :
3     def __init__ (self, name) :
4         self.name = name
5     def evaluate (self) : return
```

## AND Gate

```
1 # =====
2 # CLASS : GATE2 (2 INPUTS, 1 OUTPUT GATES)
3 # =====
4 class Gate2 (LG) :          # two input gates. Inputs A and B. Output C.
5     def __init__ (self, name) :
6         LG.__init__ (self, name)
7         self.A = Connector(self,'A', activates=1)
8         self.B = Connector(self,'B', activates=1)
9         self.C = Connector(self,'C')
10
11 # =====
12 # CLASS : AND GATE (And)
13 # =====
14 class And (Gate2) :         # two input AND Gate
15     def __init__ (self, name) :
16         Gate2.__init__ (self, name)
17     def evaluate (self) : self.C.set(self.A.value and self.B.value)
```

## XOR Gate

```
1 # =====
2 # CLASS : XOR GATE (Xor)
3 # =====
4 class Xor (Gate2) :
5     def __init__ (self, name) :
6         Gate2.__init__ (self, name)
7         self.A1 = And("A1") # See circuit drawing to follow connections
8         self.A2 = And("A2")
9         self.I1 = Not("I1")
10        self.I2 = Not("I2")
11        self.O1 = Or ("O1")
12        self.A.connect      ([ self.A1.A, self.I2.A])
13        self.B.connect      ([ self.I1.A, self.A2.A])
14        self.I1.B.connect ([ self.A1.B ])
15        self.I2.B.connect ([ self.A2.B ])
16        self.A1.C.connect ([ self.O1.A ])
17        self.A2.C.connect ([ self.O1.B ])
18        self.O1.C.connect ([ self.C ])
```



## T Flip Flop

```
1 # =====
2 # T - FlipFlop
3 # =====
4
5 class TFlipFlop (LG):
6
7     def __init__(self, name):
8         LG.__init__(self,name)
9         self.T = Connector(self,'T')
10        self.Q = Connector(self,'Q')
11        self.C = Connector(self,'C', activates = 1)
12        self.Q.value = 0
13        self.prev = 0
14
15    def evaluate (self):
16        if (not self.C.value) and self.prev and self.T.value: # clock drop and T=1
17            self.Q.set(not self.Q.value)
18        self.prev = self.C.value
```

# Example Circuit Simulation - Circuit


 


Figure: Example - 4 Bit synchronous binary counter

# Example Circuit Simulation - Code

```
1 # A 4 Bit Synchronous Binary Counter using JK Flip Flops
2 from libpydlcs import *
3
4 sim = SIMU('sim1',start = 0,plots = 1, debug =1, pclk = 1 , step =0, clocks=33)
5
6 C0 = ConstSrc('CS',value =1)
7
8 O1 = Ostream('OUT1', stream = 1)
9 O2 = Ostream('OUT2', stream = 1)
10 O3 = Ostream('OUT3', stream = 1)
11 O4 = Ostream('OUT4', stream = 1)
12
13 JK1 = JKFlipFlop('JK1')
14 JK2 = JKFlipFlop('JK2')
15 JK3 = JKFlipFlop('JK3')
16 JK4 = JKFlipFlop('JK4')
17
18 A1 = And('A1')
19 A2 = And('A2')
20
21 sim.clk_out.connect([JK4.C, O4.clk_in, JK3.C, O3.clk_in, JK2.C, O2.clk_in,C0.clk_in, JK1.C, O1.clk_in])
22 C0.data_out.connect([JK1.J, JK1.K])
23 JK1.Q.connect([JK2.J, JK2.K, A1.A, O1.data_in])
24 JK2.Q.connect([A1.B, O2.data_in])
25 A1.C.connect([JK3.J, JK3.K, A2.A])
26 JK3.Q.connect([A2.B, O3.data_in])
27 A2.C.connect([JK4.J, JK4.K])
28 JK4.Q.connect([O4.data_in])
29
30 sim.addplot([O1.data, O2.data, O3.data, O4.data])
31 sim.addpname(["Q1", "Q2", "Q3", "Q4"])
32
33 sim.start = 1
34 sim.simulate()
```

## Example Circuit Simulation - Plots

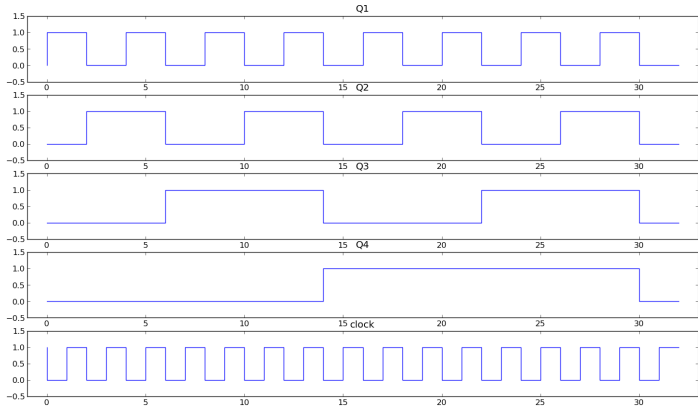

**Figure:** Example - 4 Bit synchronous binary counter plot

## Project Status

- Project status - Complete as per proposal
- Work hours put - approximately 25 hours per person

## Project Status

- Project status - Complete as per proposal
- Work hours put - approximately 25 hours per person

## Future Work

- GUI is not provided completely, so this could be potential future work.
- Feedback that activates the evaluation function is not possible in current release, this problem could be rectified.

Thank You !